


Designing a Single Cycle Datapath

or

The Do-It-Yourself CPU Kit

The Big Picture: Where are We Now?

 - The Five Classic Components of a Computer




- Today's Topic: the ALU and Datapath Design, next topic Control Design


The Big Picture: The Performance Perspective

- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Starting today:
 - Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

- $ET = Insts * CPI * Cycle\ Time$

 

Clocking Methodology

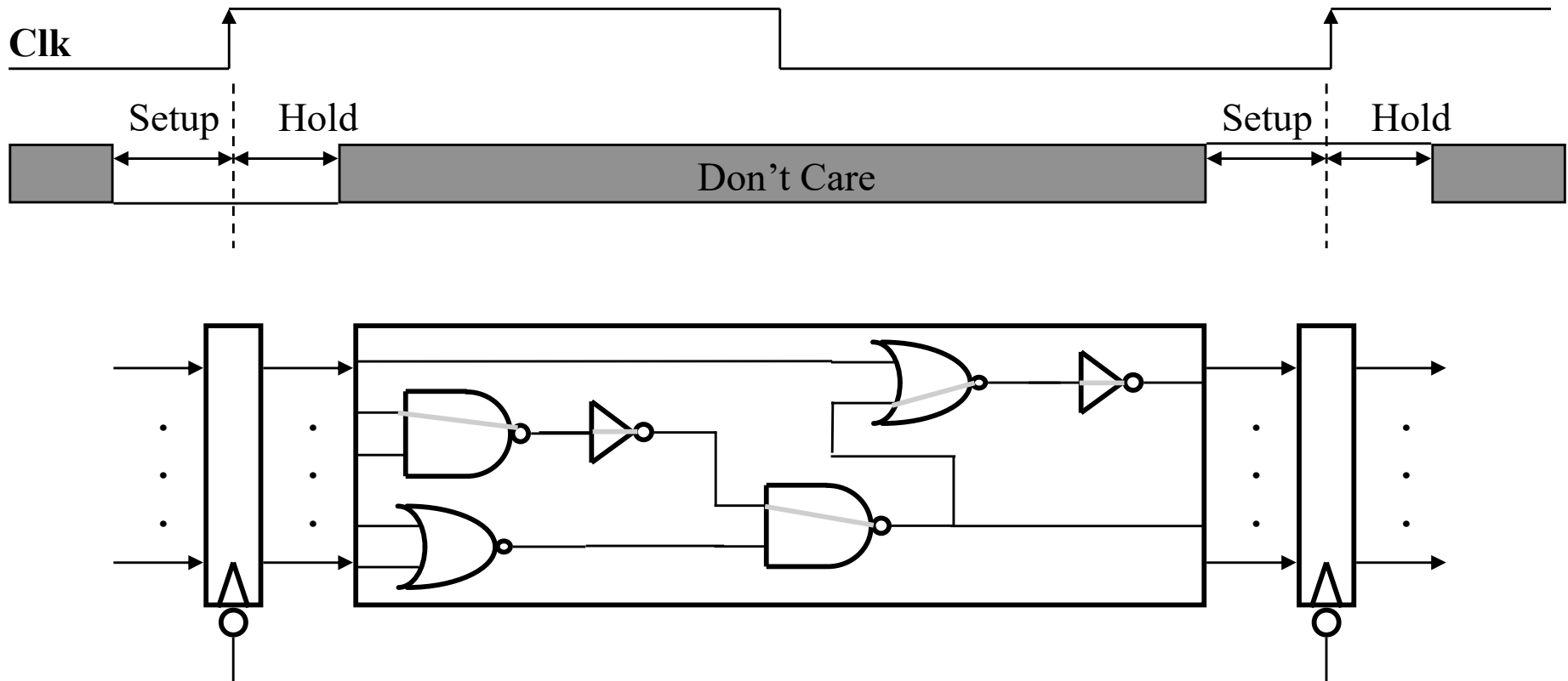


- All storage elements are clocked by the same clock edge
- This picture is valid whether we're talking about a single-cycle processor, multi-cycle processor, pipelined processor, ...

The Processor: Datapath & Control

- We're going to look at an implementation of MIPS simplified to contain only:
 - memory-reference instructions: `lw, sw`
 - arithmetic-logical instructions: `add, sub, and, or, slt`
 - control flow instructions: `beq`
- Generic Implementation:
 - use the `program counter (PC)` to supply instruction address
 - get the `instruction` from memory
 - read registers
 - use the instruction to decide exactly what to do

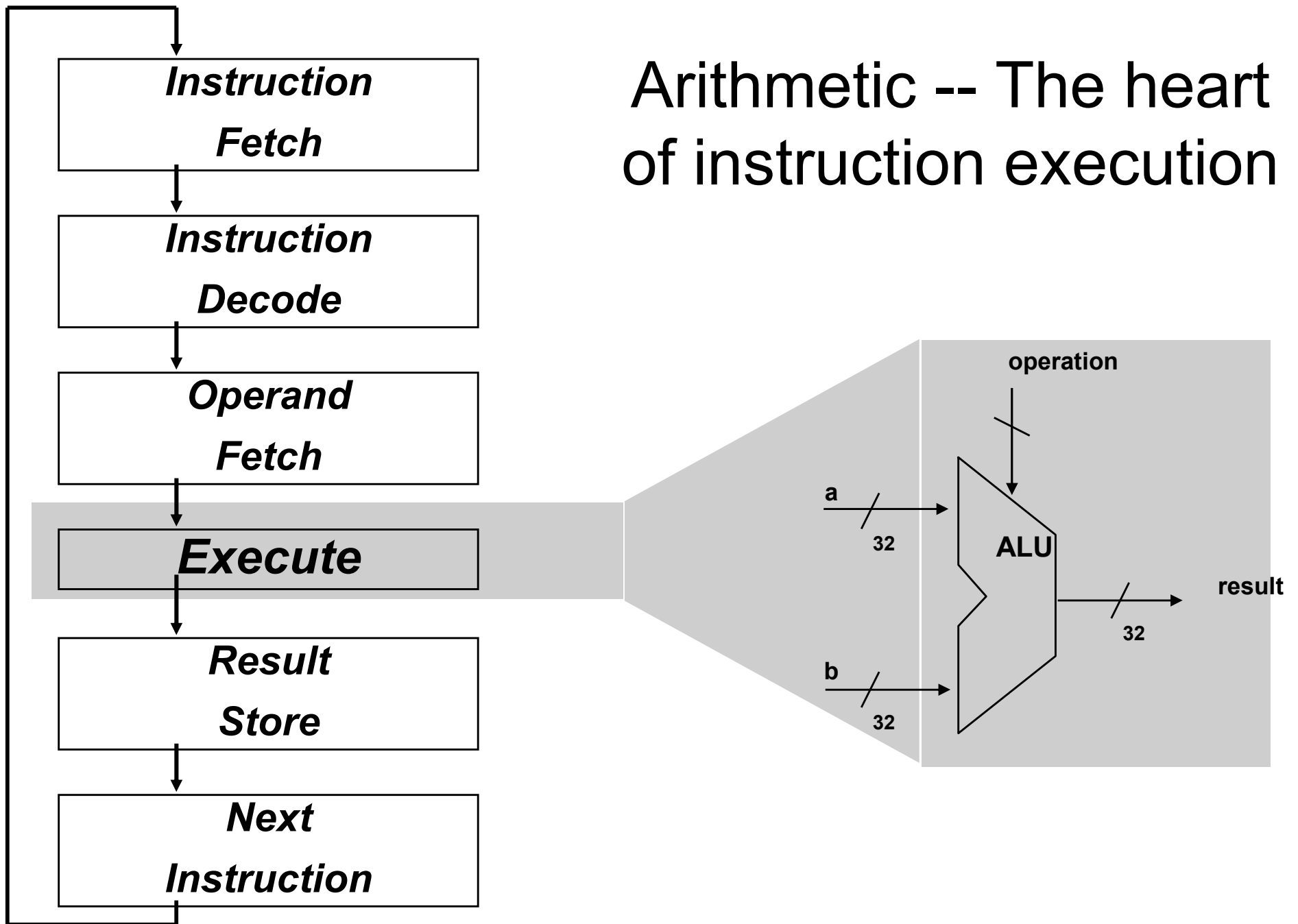Arithmetic -- The heart of instruction execution



Computer Arithmetic

- We're going to go over this pretty fast, but it shouldn't be very much you haven't seen before.

Okay, let's stop and recall a little math...

Recall: 2's complement

- We would like a *number system* that provides
 - obvious representation of 0,1,2...
 - uses an adder for both unsigned and signed addition
 - single value of 0
 - equal coverage of positive and negative numbers
 - easy detection of sign
 - easy negation

Two's Complement Representation

- 2's complement representation of negative numbers
 - Take the bitwise inverse and add 1
- Biggest 4-bit Binary Number: 7 Smallest 4-bit Binary Number: -8

<u>Decimal</u>	<u>Two's Complement Binary</u>
-8	1000
-7	1001
-6	1010
-5	1011
-4	1100
-3	1101
-2	1110
-1	1111
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111

Two's Complement Arithmetic

Decimal	2's Complement Binary	Decimal	2's Complement Binary
0	0000	-1	1111
1	0001	-2	1110
2	0010	-3	1101
3	0011	-4	1100
4	0100	-5	1011
5	0101	-6	1010
6	0110	-7	1001
7	0111	-8	1000


- Examples: $7 + (-6) = 1$

$$\begin{array}{r} \\ \\ + \\ \hline \end{array}$$

$$3 + (-5) = -2$$

$$\begin{array}{r} \\ \\ + \\ \hline \end{array}$$



Designing an Arithmetic Logic Unit

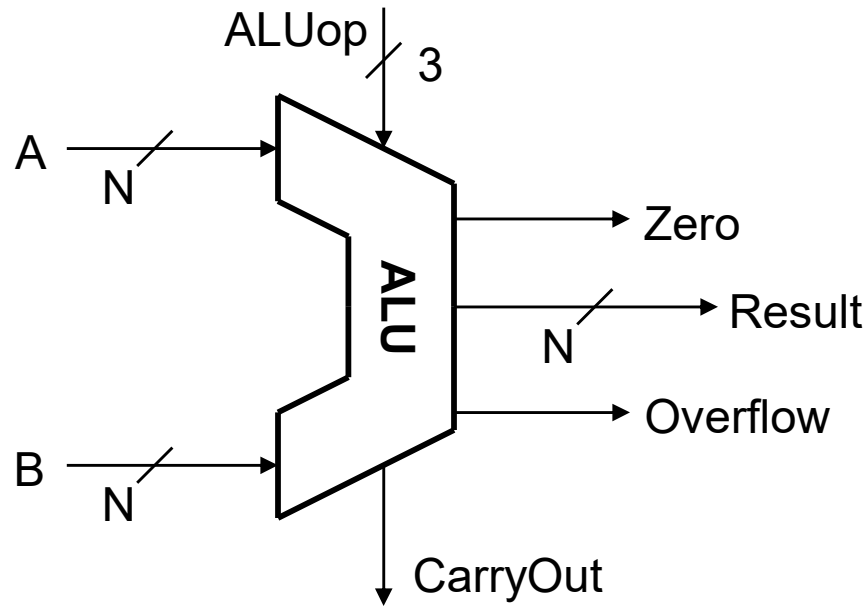

- | <u>ALU Control Lines (ALUOp)</u> | <u>Function</u> |
|----------------------------------|------------------|
| – 000 | And |
| – 001 | Or |
| – 010 | Add |
| – 110 | Subtract |
| – 111 | Set-on-less-than |


A One Bit ALU

  - This 1-bit ALU will perform AND, OR, and ADD for a single bit position.




A 32-bit ALU

1-bit ALU

 


32-bit ALU

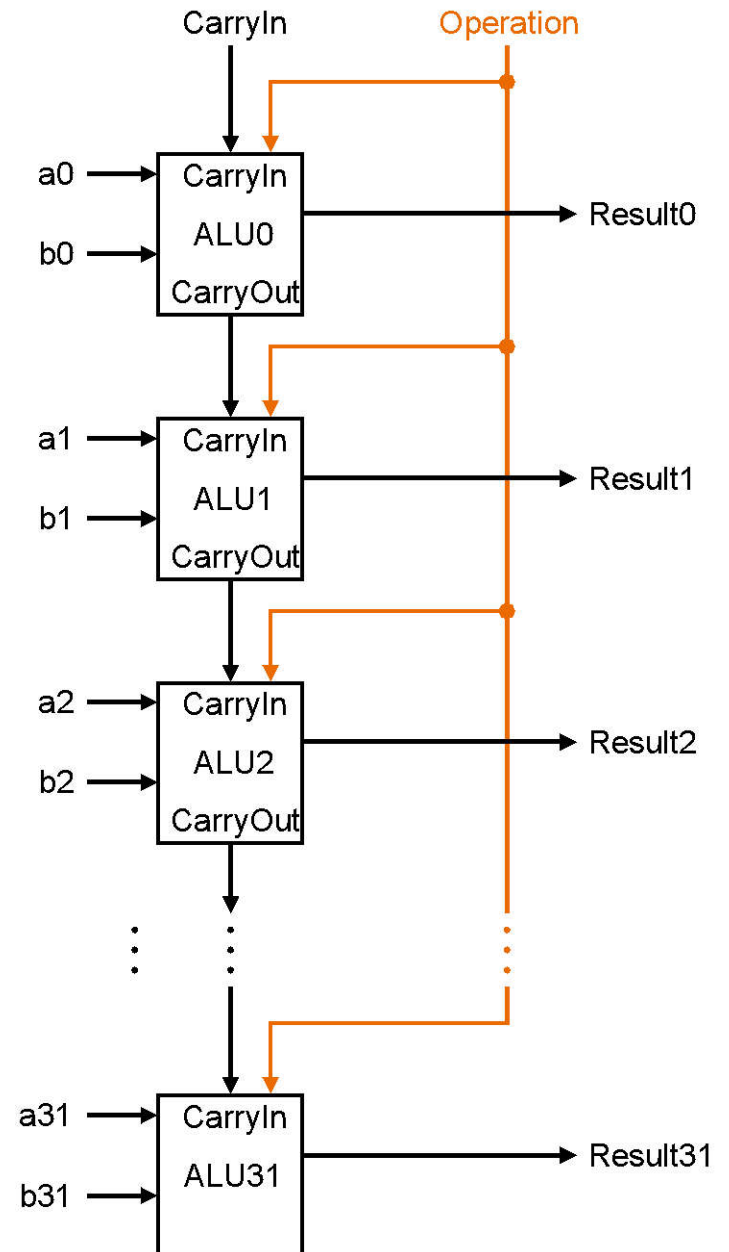

How About Subtraction?

 - Keep in mind the following:
 - $(A - B)$ is the same as: $A + (-B)$
 - 2's Complement negate: Take the inverse of every bit and add 1
- Bit-wise inverse of B is $\neg B$:
 - $A - B = A + (-B) = A + (\neg B + 1) = A + \neg B + 1$
 - How does this help us?




$$\begin{array}{r} 1 \\ + \\ \hline 0 \end{array}$$



The diagram shows a 4-bit subtraction operation: $1010 - 0101$. The result is 0101 . The carry bits are shown as 1, 0, 1, 0 from left to right, indicating the borrow chain.

Full ALU

a.

 

b.


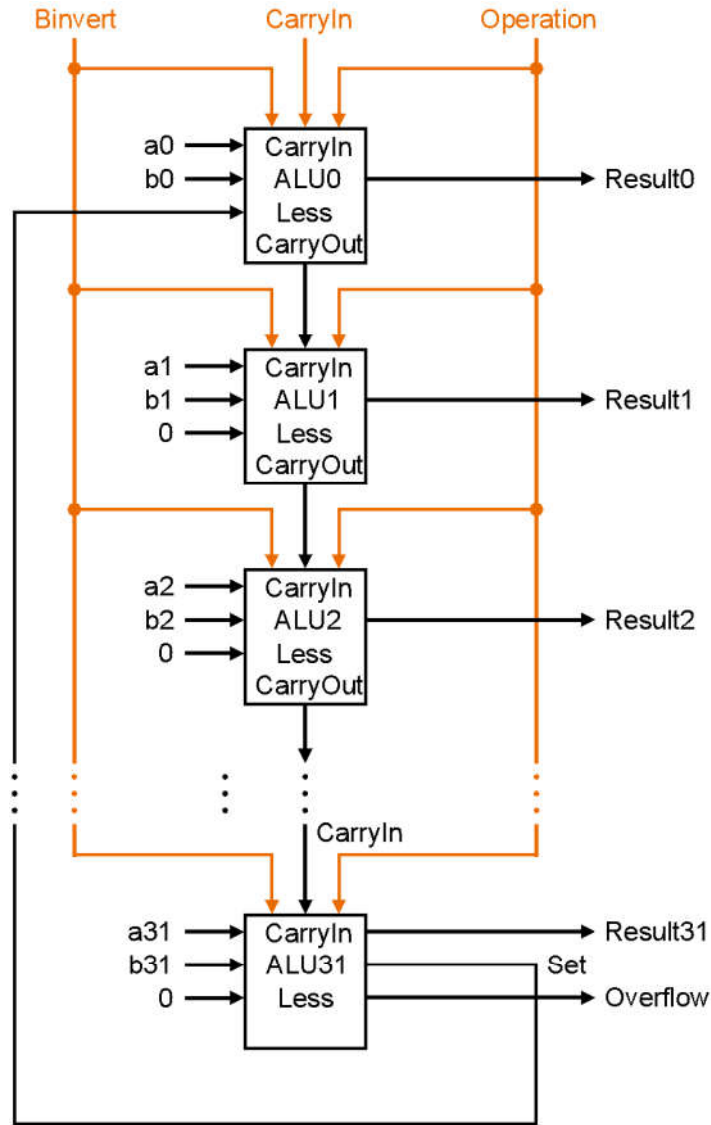
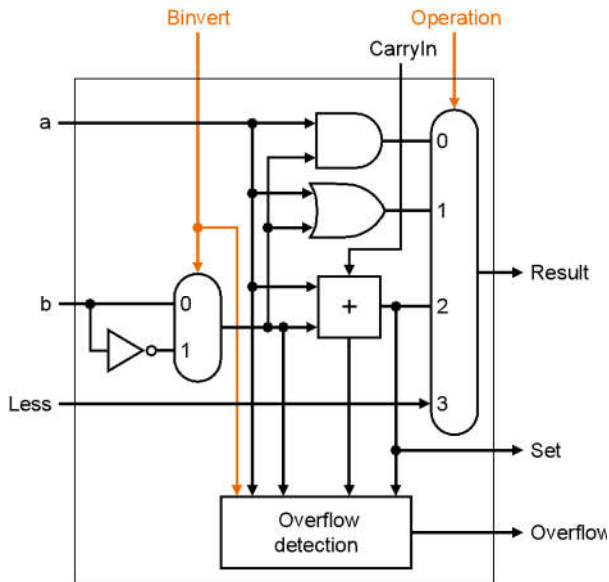


sign bit (adder output from bit 31)

what signals accomplish ADD?

	<u>Binvert</u>	<u>CIn</u>	<u>Oper</u>
A	1	0	2
B	0	1	2
C	1	1	2
D	0	0	2
E	NONE OF THE ABOVE		

Full ALU

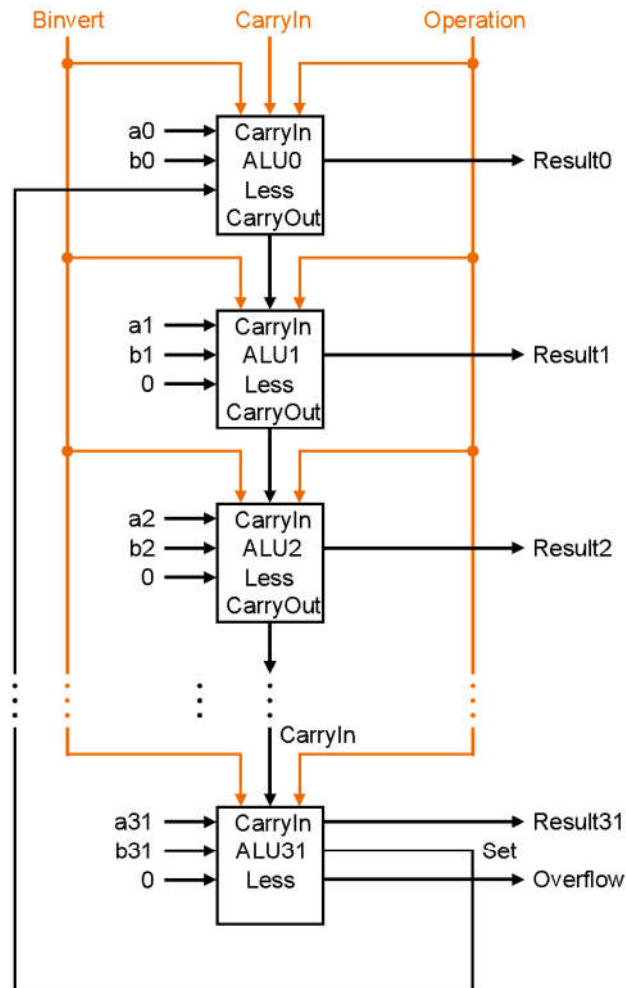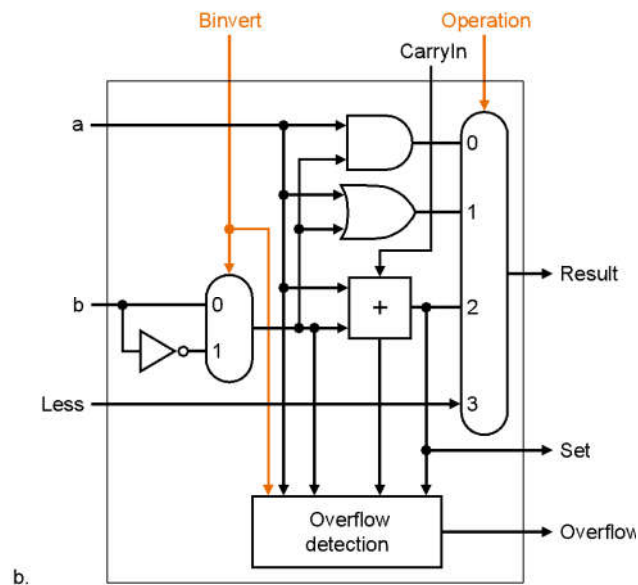 

sign bit (adder output from bit 31)




Recall:
`slt $t0, $t1, $t2`
 Means:
 if($\$t1 < \$t2$)
 $\$t0 = 1$
 else
 $\$t0 = 0$

Which signals accomplish SLT
 (assume A is \$t1, B is \$t2)

	Binvert	CIn	Oper	
A	1	0	2	
B	0	1	2	
C	1	1	3	
D	0	0	3	
E	NONE OF THE ABOVE			

(not a poll question – let's work it out together).

Full ALU

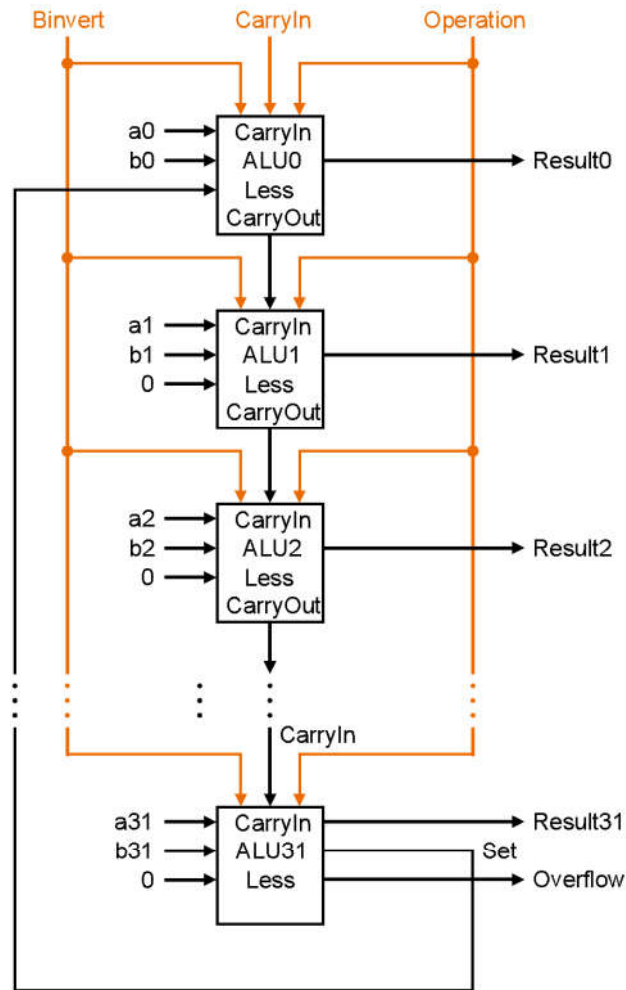  



sign bit (adder output from bit 31)

what signals accomplish?
Binvert CIn Oper

add?
 sub?
 and?
 or?
 beq?
 slt?

The Disadvantage of Ripple Carry

 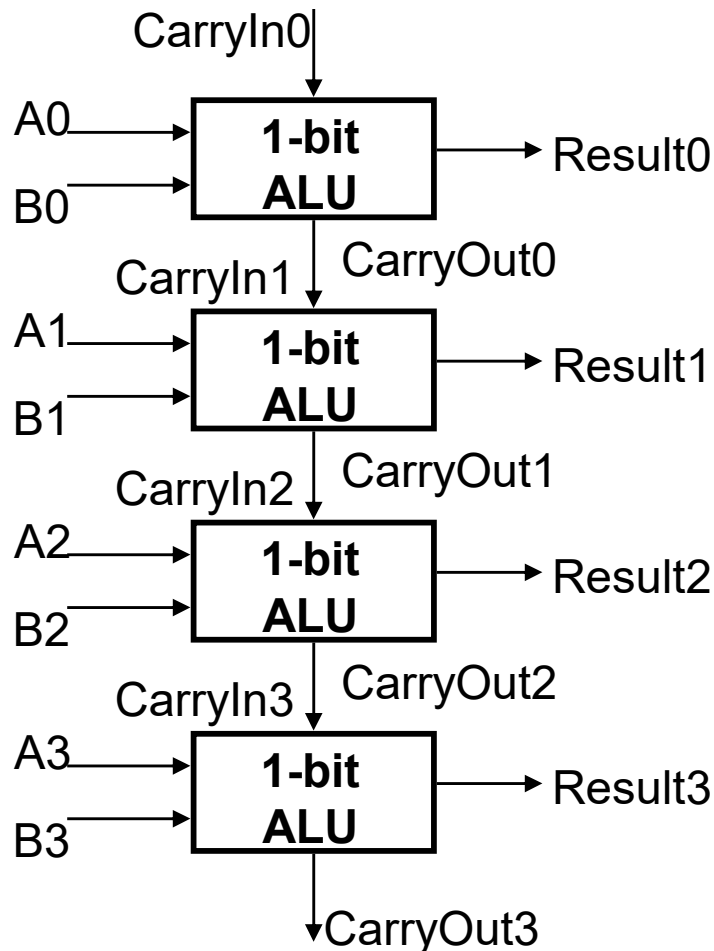
- The adder we just built is called a “Ripple Carry Adder”
 - The carry bit may have to propagate from LSB to MSB
 - Worst case delay for an N-bit RC adder: $2N$ -gate delay



The point -> ripple carry adders are slow. Faster addition schemes are possible that *accelerate* the movement of the carry from one end to the other.

MULTIPLY HARDWARE

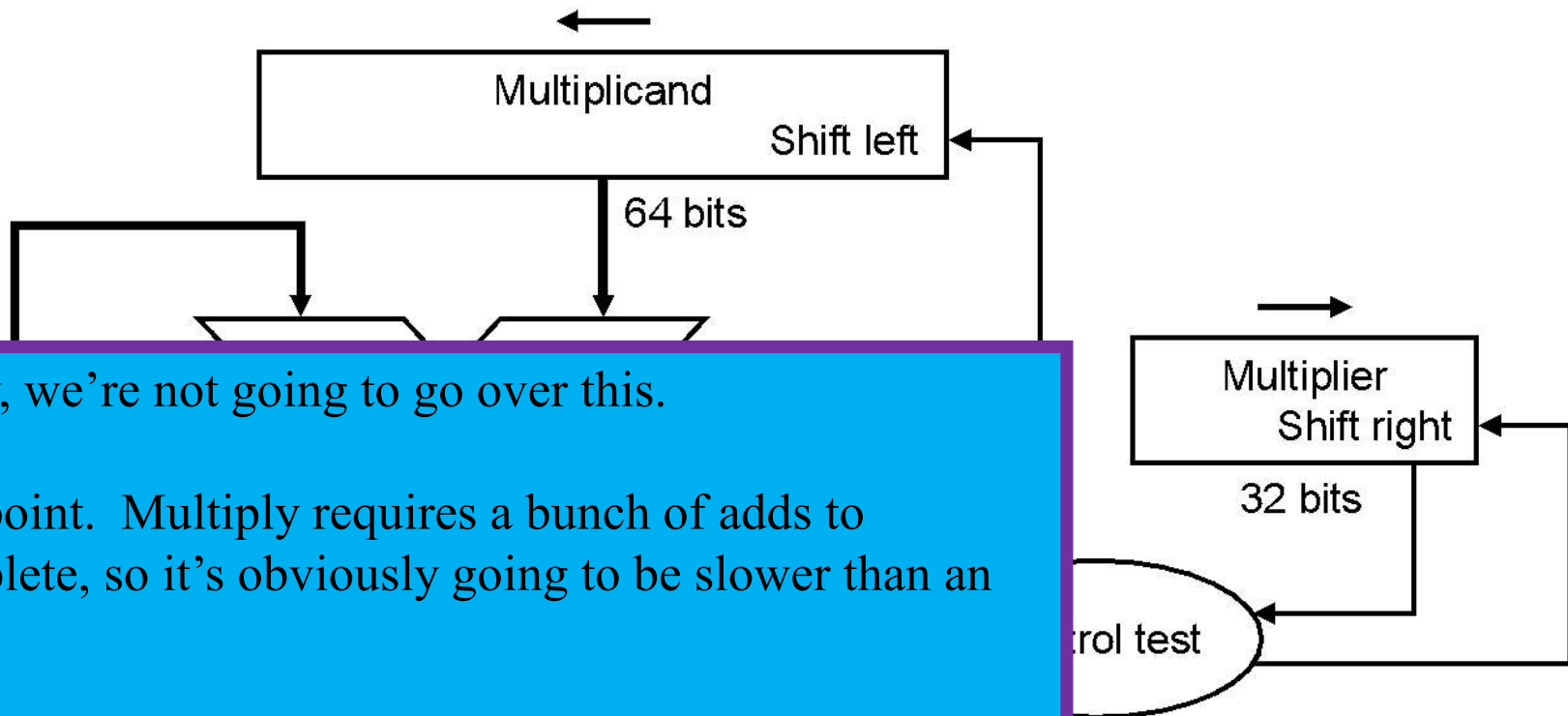- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg




Okay, we're not going to go over this.

Big point. Multiply requires a bunch of adds to complete, so it's obviously going to be slower than an add.

Divide is similar, but worse.

Floating-Point Numbers

 Representation of floating point numbers in IEEE 754 standard:



sign *exponent*

mantissa:

Okay, how much do we remember about floating point numbers? Do we really need to go over this?


Maybe just some high level points?

le, normalized
and w/ hidden
bit: 1.M

Floating Point

- Typically will have their own ALU (and register file!)
- Because they require normalization, then math, then renormalization, then rounding (a lot of **serialized** steps)...
- FP computations are always slower than integer.
 - Eg, Skylake
 - Int add 1, int mul 4, FP add 3, FP mul 5

- Okay, now that we have an ALU...

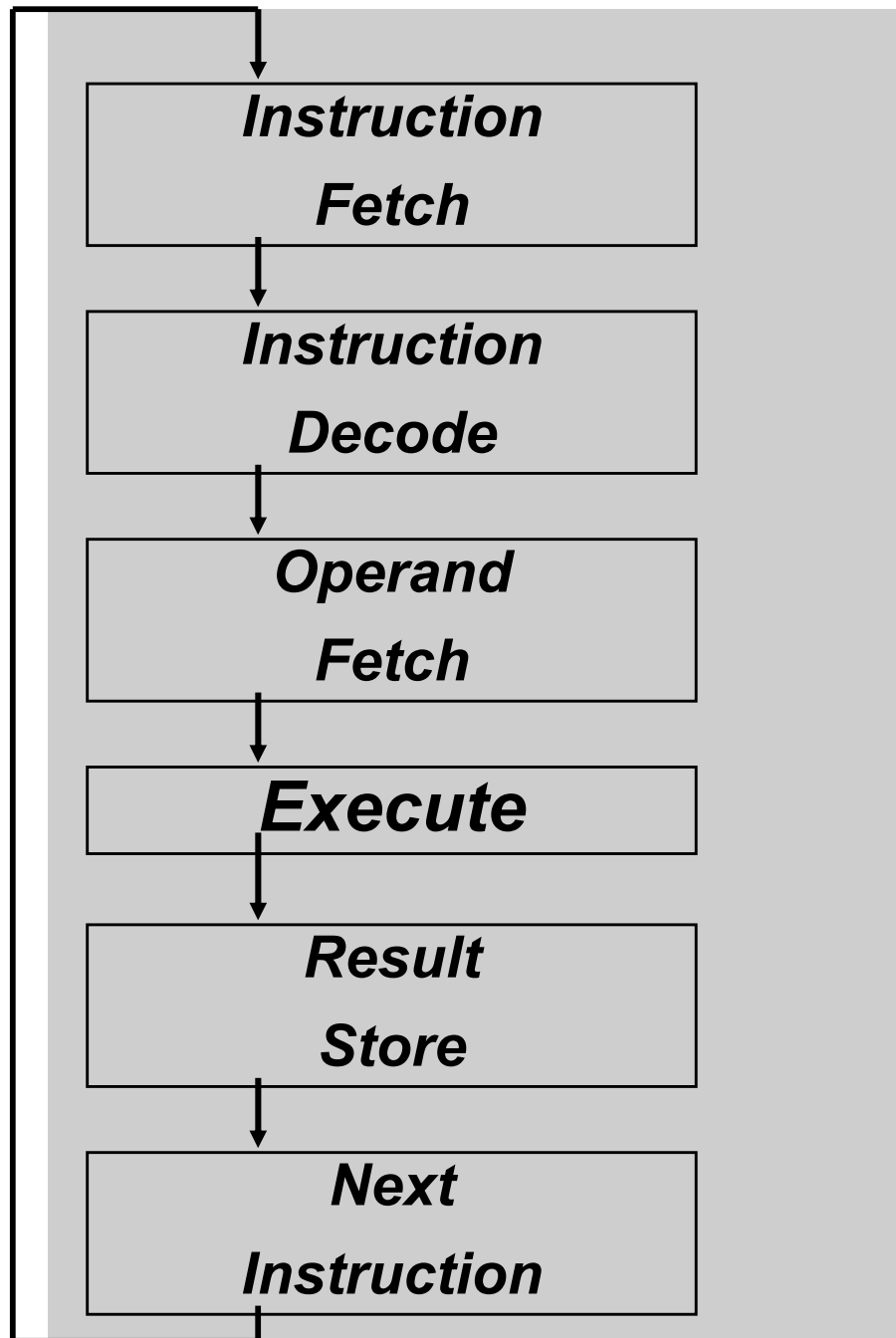

Let's look beyond just
Execute now.

Register Transfer Language (RTL)

- is a mechanism for describing the movement and manipulation of data between storage elements:

$R[3] \leftarrow R[5] + R[7]$


$PC \leftarrow PC + 4 + R[5]$

$R[rd] \leftarrow R[rs] + R[rt]$

$R[rt] \leftarrow Mem[R[rs] + immed]$

Review: The MIPS Instruction Formats

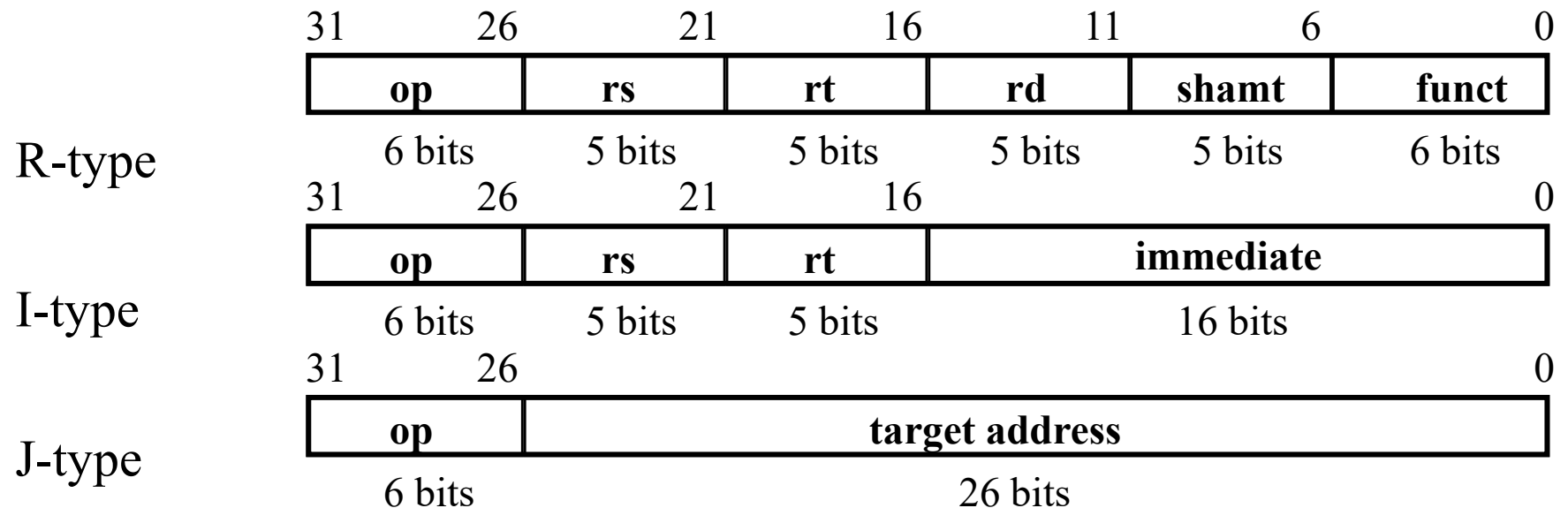
- All MIPS instructions are 32 bits long. The three instruction formats:



The MIPS Subset

- R-type**

- *add rd, rs, rt*
- *sub, and, or, slt*

 


$PC = PC + 4$

$R[rd] = R[rs] \text{ OP } R[rt]$

- LOAD and STORE**

 - *lw rt, rs, imm16*
- *sw rt, rs, imm16*




$PC = PC + 4$

$R[rt] = \text{Mem}[R[rs] + \text{SE}(\text{imm})] \text{ OR}$

$\text{Mem}[R[rs] + \text{SE}(\text{imm})] = R[rt]$

- BRANCH:**

- *beq rs, rt, imm16*

 

$\text{ZERO} = (R[rs] - R[rt] == 0)$

$PC = \text{if}(\text{ZERO}) \quad PC + 4 + (\text{SE}(\text{Imm}) \ll 2)$


Else $PC = PC + 4$

Storage elements

- RTL describes data movement between storage elements, but we don't actually have our data elements yet.
- So...

Storage Element: Register

 
- Register
 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
 - Write Enable:
 - 0: Data Out will not change
 - 1: Data Out will become Data In (on the clock edge)
- But we need a whole bunch of registers
 - Register File




Reg File



Register File

 


Memory

 


Can we layout a high-level design to do all this
now?

Putting it All Together: A Single Cycle Datapath

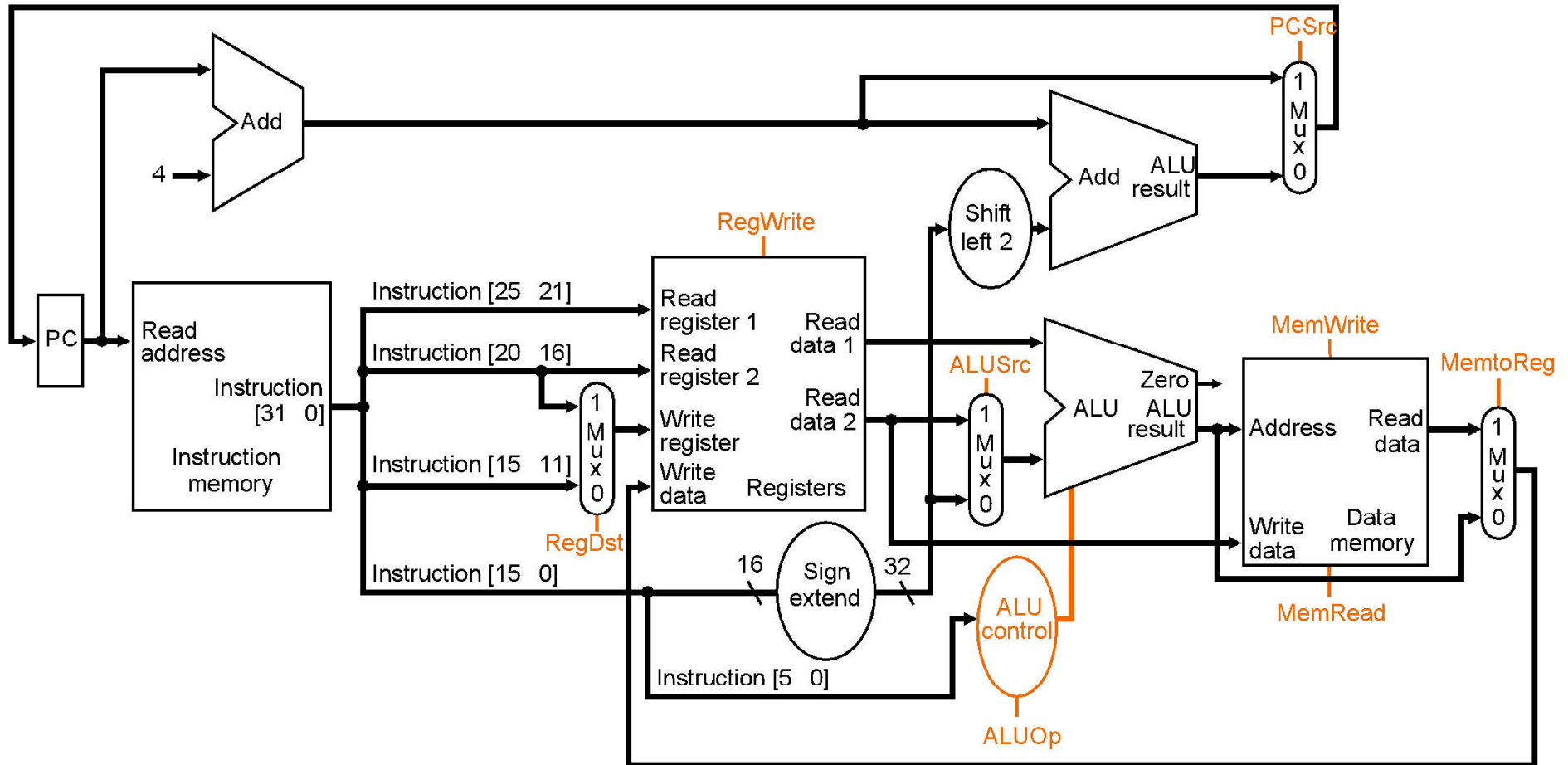
- We have everything except control signals (later)



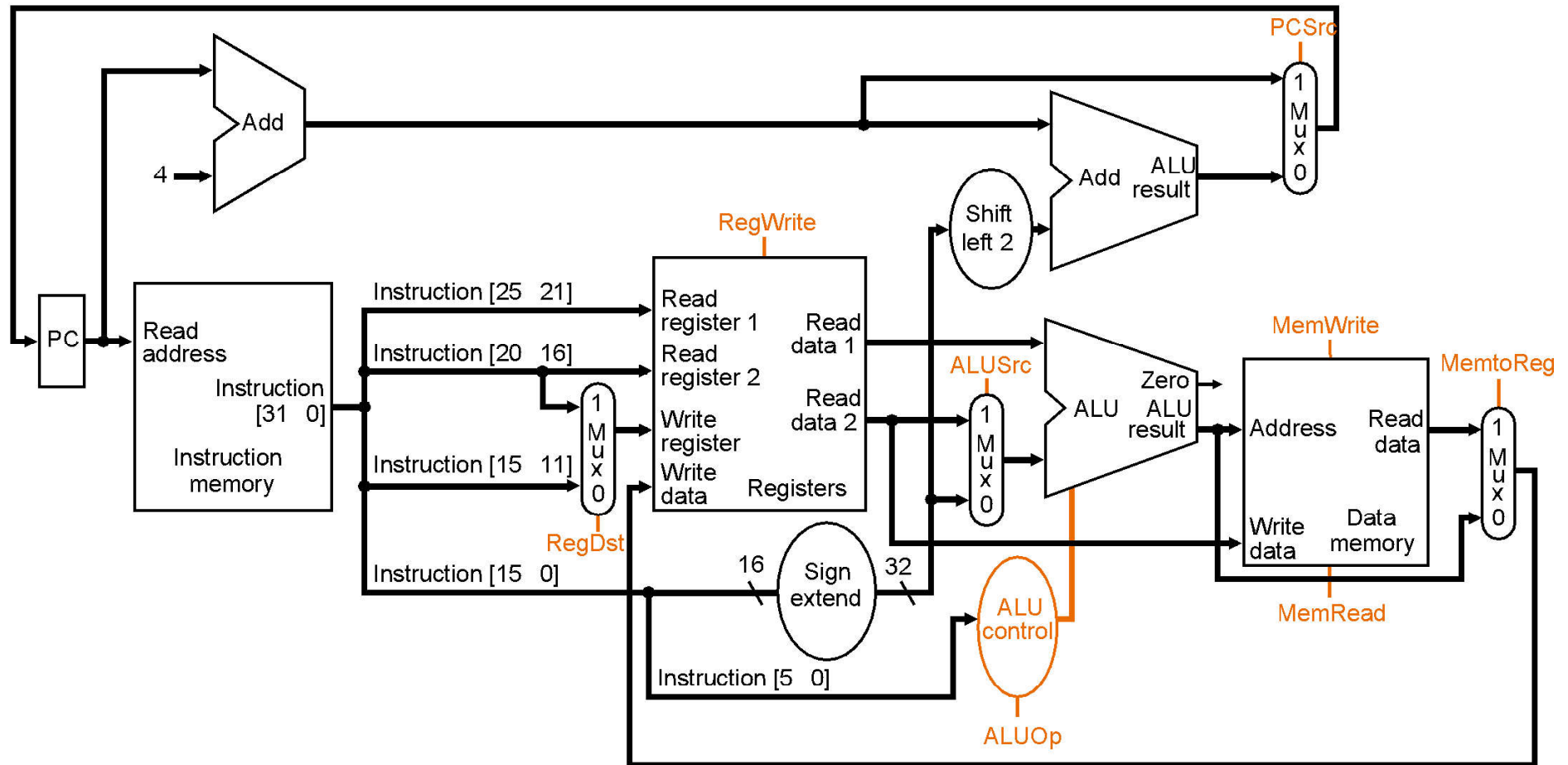How do we make this execute an R-type instruction?




Active Single-Cycle Datapath

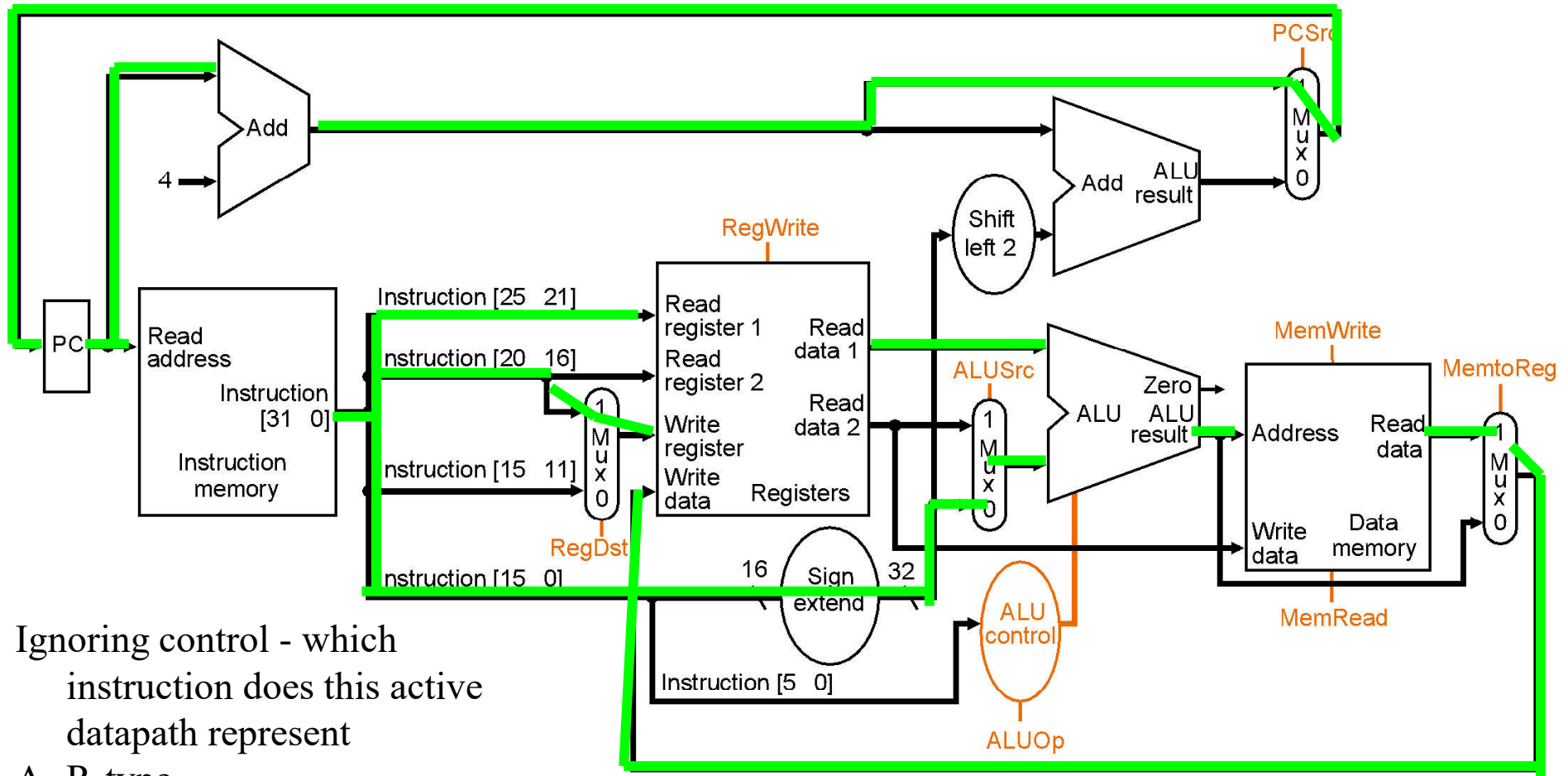

Ignoring control - which instruction does this active datapath represent

- A. R-type
- B. lw
- C. sw
- D. Beq
- E. None of the above


Active Single-Cycle Datapath

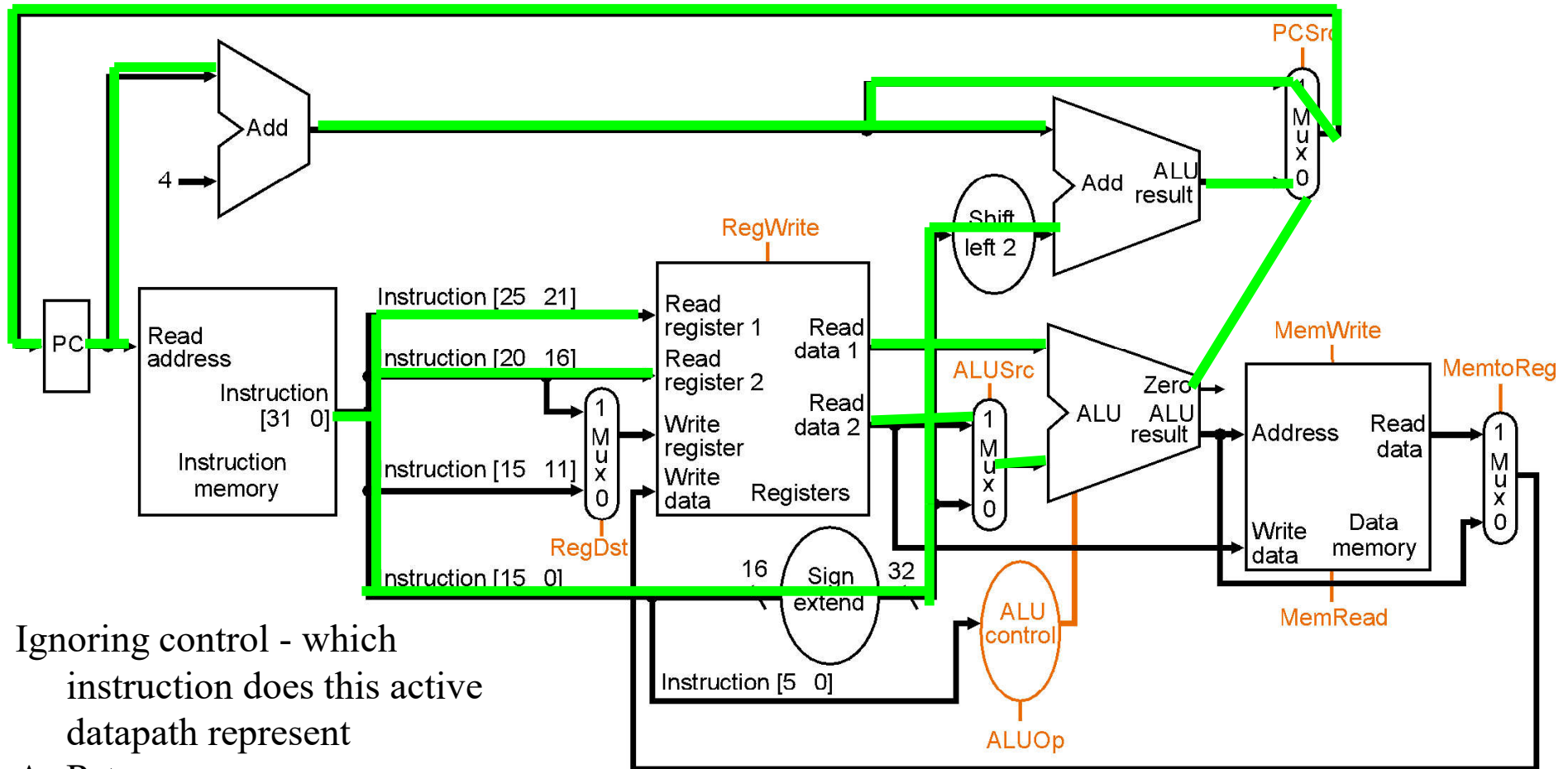

Ignoring control - which instruction does this active datapath represent

- A. R-type
- B. lw
- C. sw
- D. Beq
- E. None of the above

Active Single-Cycle Datapath

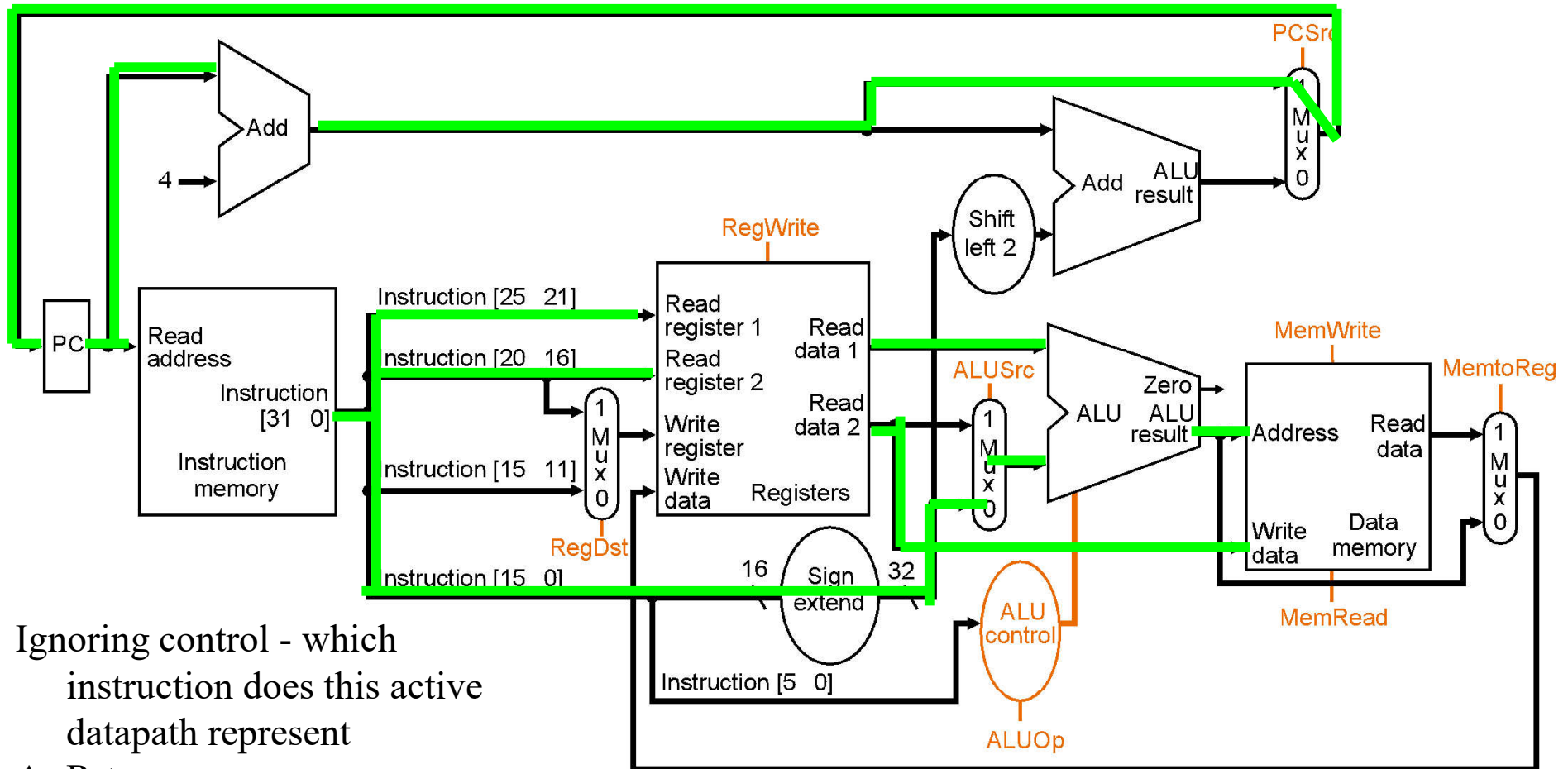

Ignoring control - which instruction does this active datapath represent

- A. R-type
- B. lw
- C. sw
- D. Beq
- E. None of the above

Key Points

- CPU is just a collection of state and combinational logic
- We just designed a the datapath for a very rich processor, at least in terms of functionality
- $ET = IC * CPI * \text{Cycle Time}$
 - where does the single-cycle machine fit in?